

Bangladesh University of Engineering and Technology

Department of Electrical and Electronic Technology

EEE 428

Measurement and Instrumentation Laboratory

Experiment 4

Signal Processing: Precision Rectification

Name: Md Maisoon Rahman

Student ID: 1606038

Level: 4, Term: 1

Dept. EEE

Measurement and Instrumentation Laboratory

EEE 428

Experiment No :04

Experiment Title : Signal Processing: Precision Rectification

Objective :

In this report, the aim is to measure AC Voltage sources through integrated circuits.

Setup:

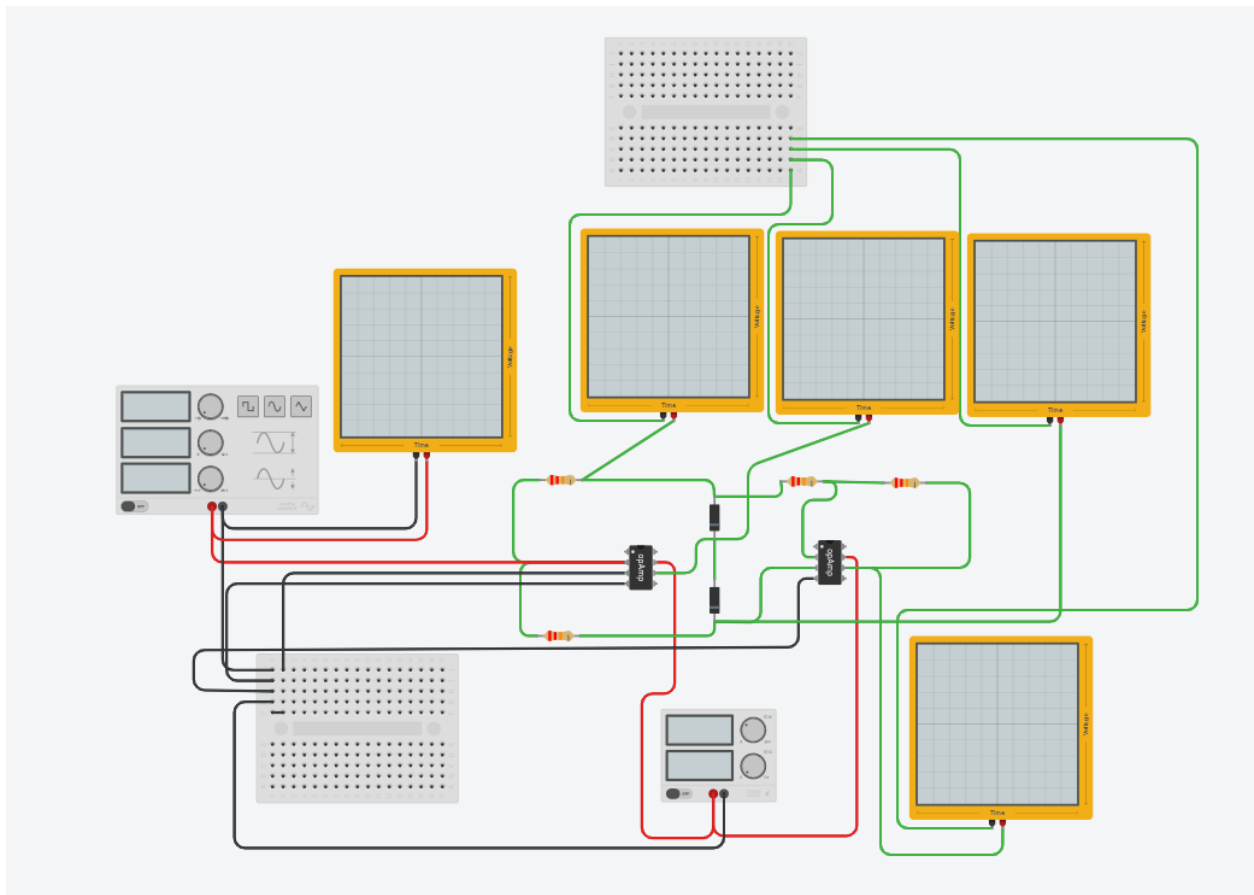


Figure 1 Tinkercad simulation circuit diagram

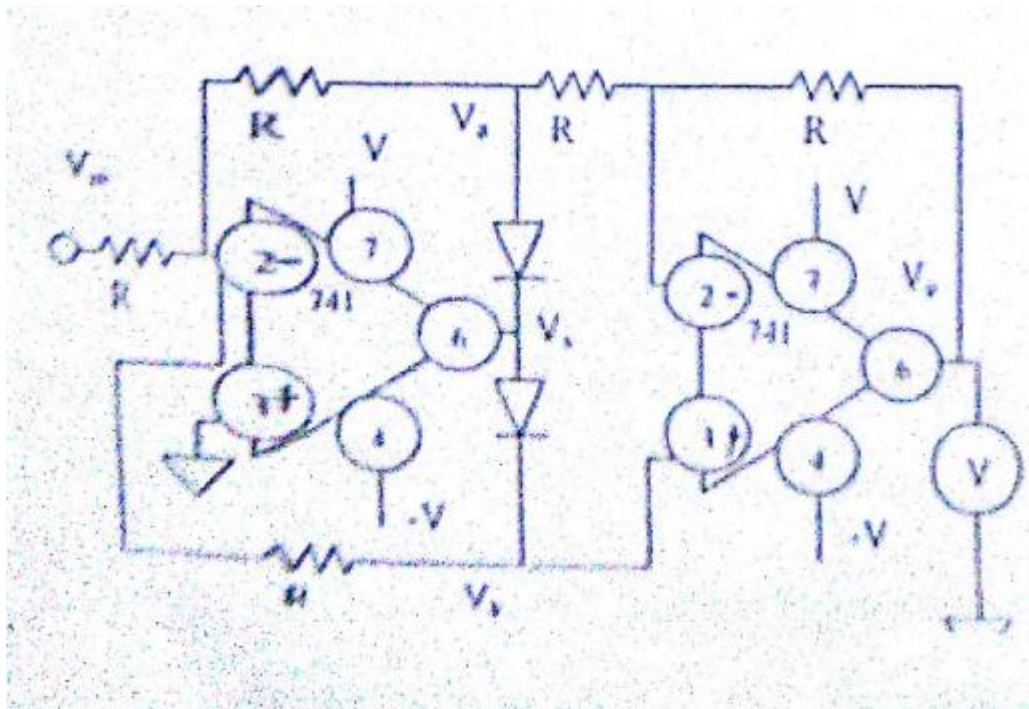


Figure 2 Circuit Diagram

The tinker cad simulation after simulating:


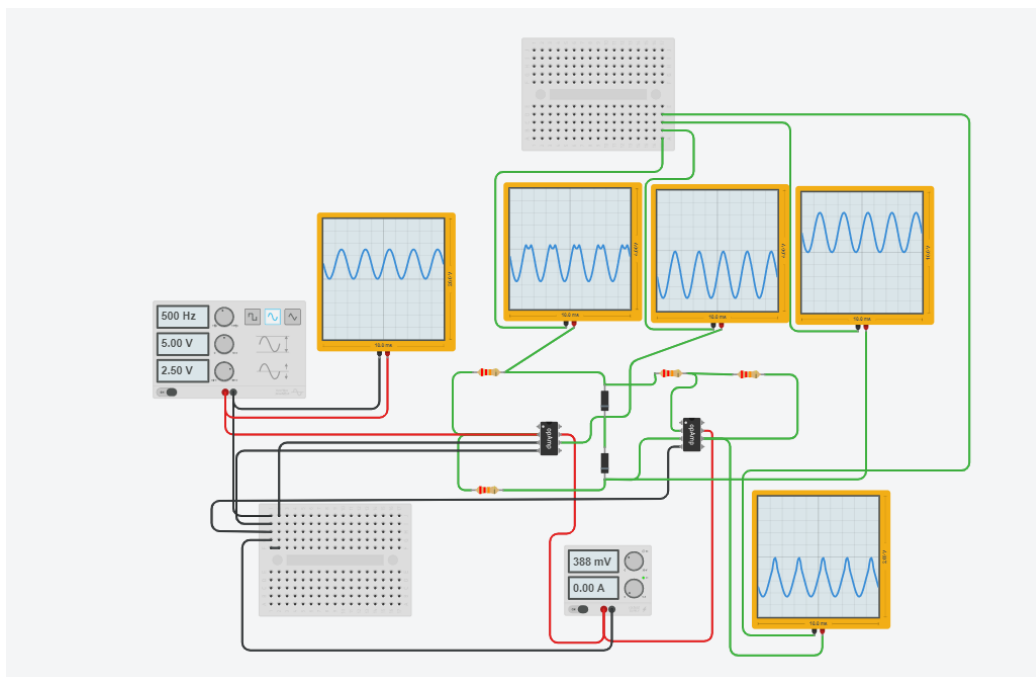


Figure 3 Simulated circuit


The following outputs were observed for V_{in} , V_a , V_b , V_x , V_o

For Case $R = 22\text{k}\ \Omega$


V_{in}

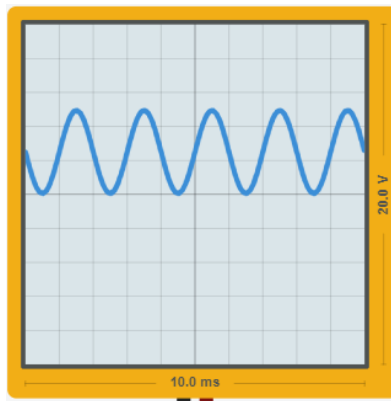


V_a

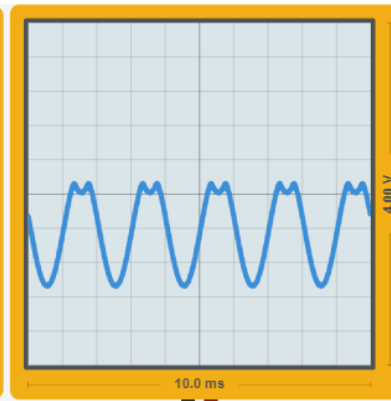


V_x

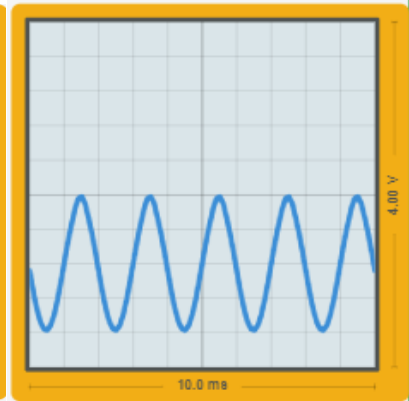

V_b

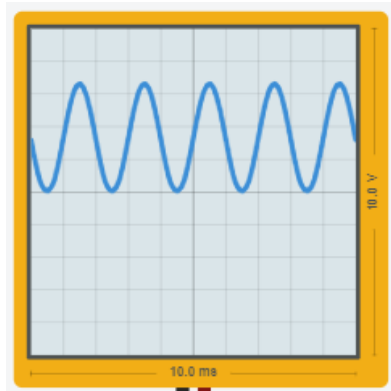


V_o

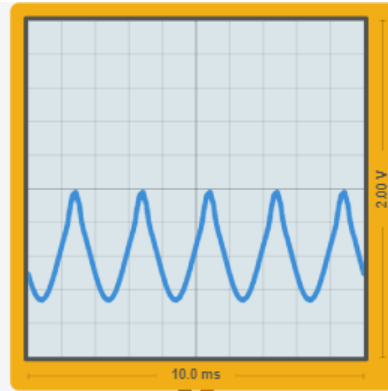


For Case $R = 10\text{k Ohm}$


V_{in}

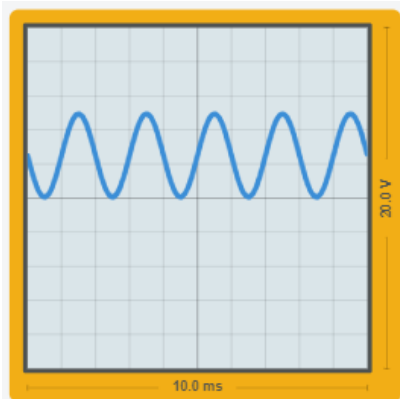


V_a

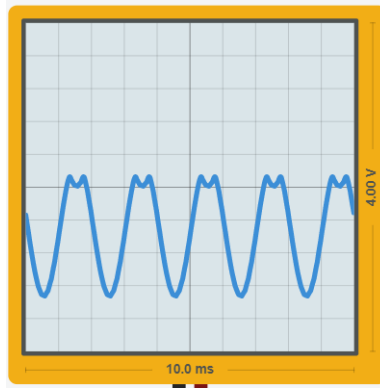


V_x

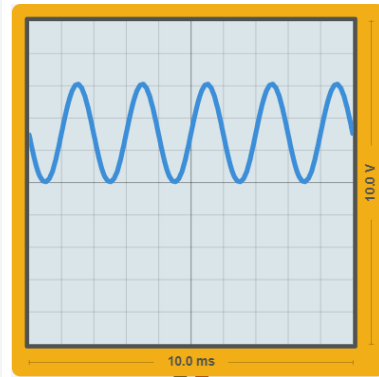

V_b

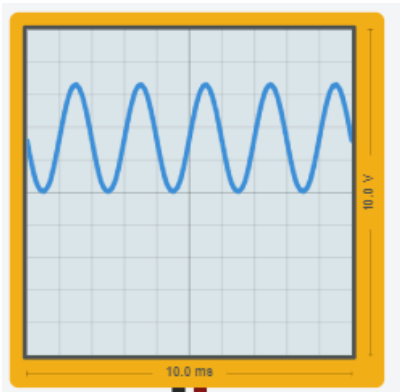


V_o

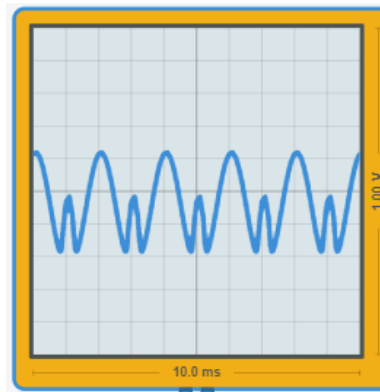


For Case $R = 100\text{k Ohm}$


V_{in}

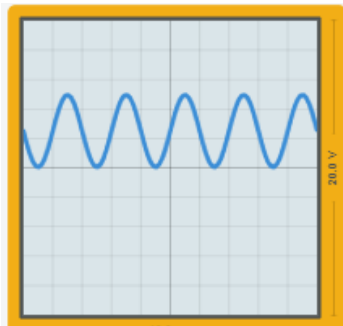


V_o

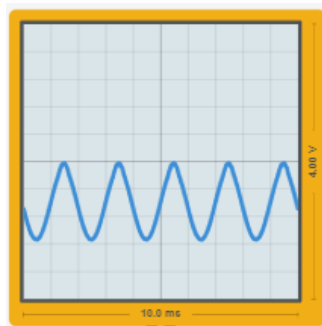


V_a

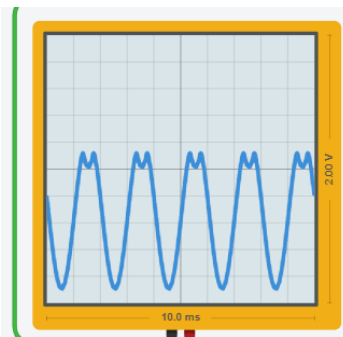

V_x

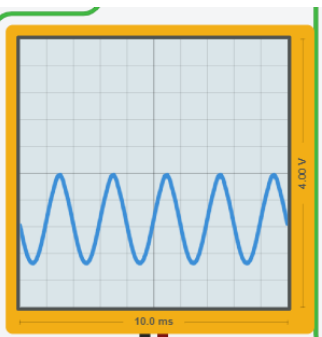


V_b

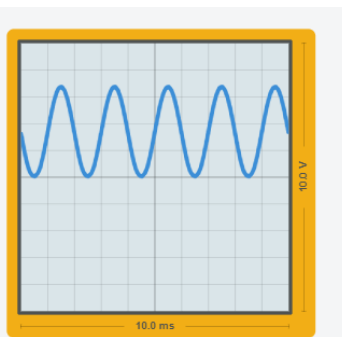


For Case $R = 220\text{k Ohm}$


V_{in}

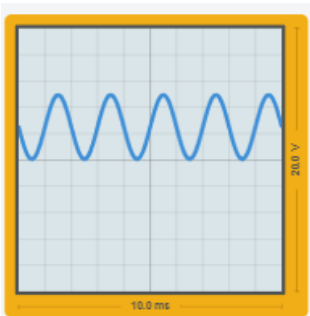


V_o

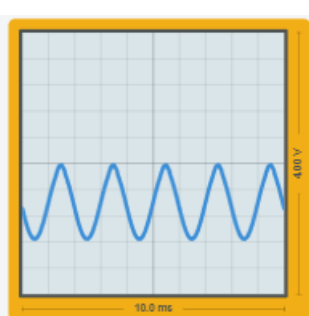


Va

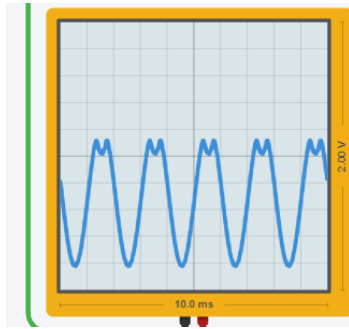

Vx

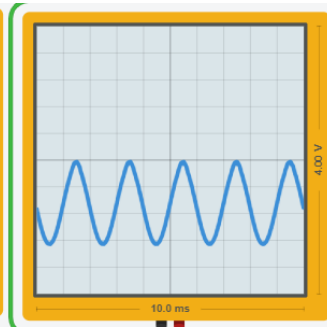

Vb

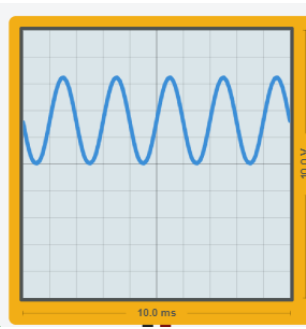

Conclusion :

Throughout the experiment, the full wave rectification of an ac voltage was observed.