

Bangladesh University of Engineering and Technology

Department of Electrical and Electronic Technology

EEE 428

Measurement and Instrumentation Laboratory

Experiment 2

High Resistance Measured by Loss of Charge Method

Name: Md Maisoon Rahman
Student ID: 1606038
Level: 4, Term: 1
Dept. EEE

Measurement and Instrumentation Laboratory

EEE 428

Experiment No :02

Experiment Title : High Resistance Measured by Loss of Charge Method

Objective of the experiment

Using the Loss of charge method to determine the high resistance values.

Experimental Setup:

The following circuit was implemented in Tinkercad for the experimentation.

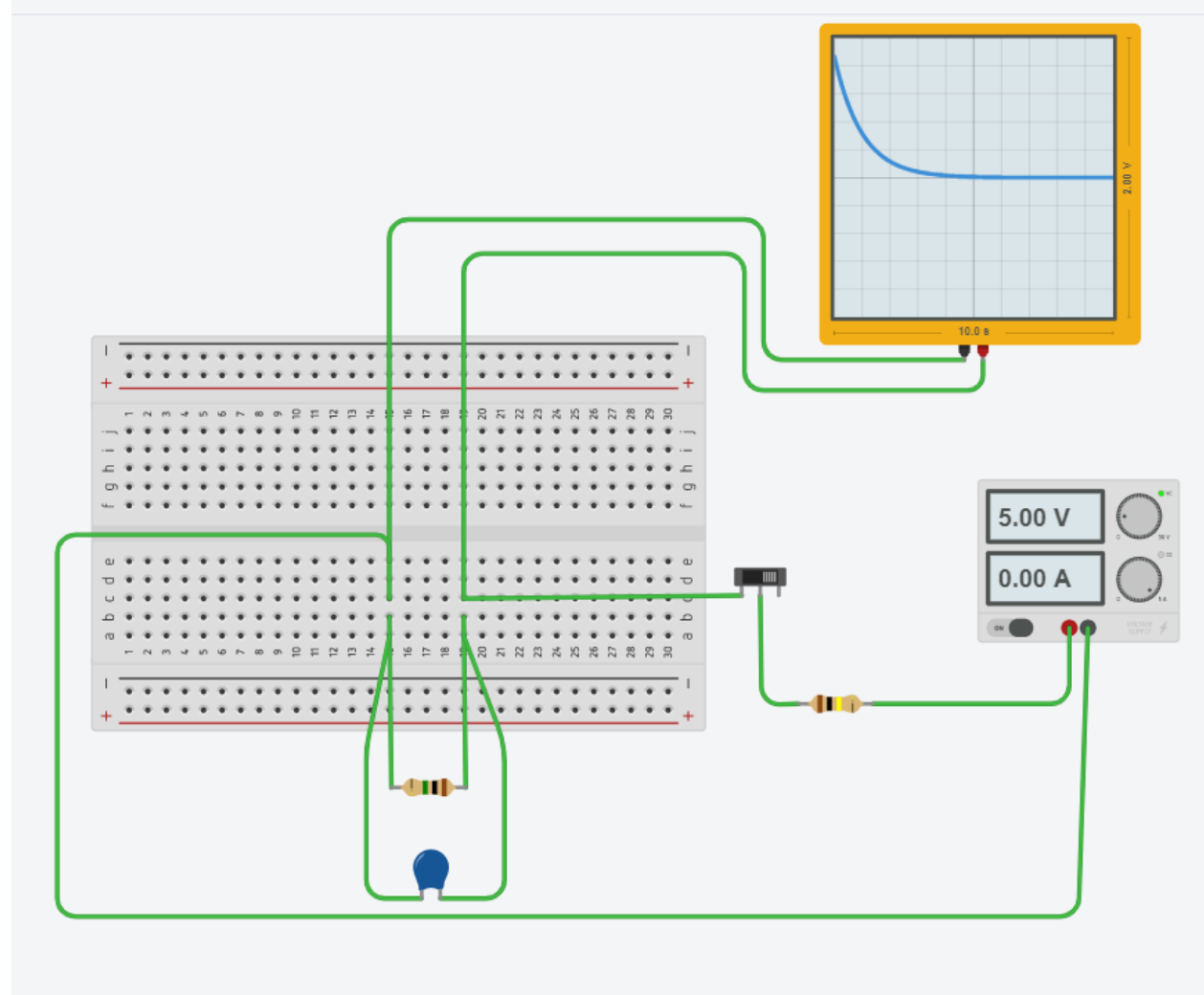


Figure 1 Tinkercad Implementation

Here, instead of a normal multimeter, we used an oscilloscope as that shows the time of voltage discharge, which is crucial for our calculation.

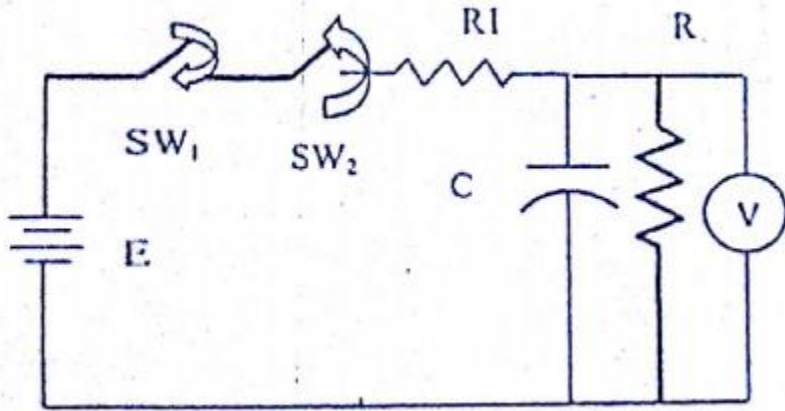


Figure 2 Schematic diagram

In our tinkercad simulation,
at first we observed the output for the following parameters :

$$C = 1\mu\text{F}$$

$$R = 1\text{M Ohm}$$

$$R_1 = 100\text{ kOhm}$$

Then, we observed the performance for the following parameters :

$$C = 10\mu\text{F}$$

Then we changed the resistance to :

$$R = 2, 4, 10\text{ M ohm}$$

The following Observations were obtained :

CASE 1 (1 μF , $R = 1\text{M Ohm}$, $R1 = 100\text{ k Ohm}$)




The Capacitor took almost 5s to discharge .

The following table was obtained :

Time	Voltage across C
t=0s	4.54 V
1s	1.5 V
2s	0.75 V
3s	0.25V
4s	0.05 V
5s	0.2 mV

Calculating, $R = t / [c \log (E/V)]$
= 1.147 M Ohm

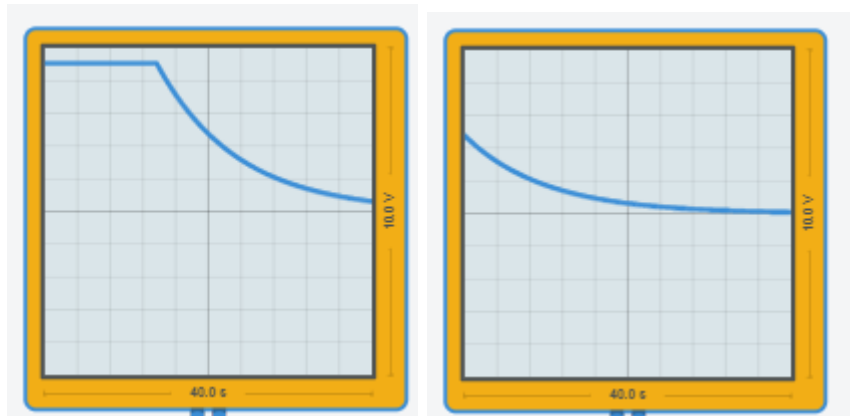CASE 2 (10uF , R = 1M Ohm, R1 = 100 k Ohm)




The Capacitor took almost 5s to discharge .

The following table was obtained :

Time	Voltage across C
t=0s	4.54 V
1s	3.5 V
2s	3 V
3s	2.4 V
4s	2 V
5s	1.6V
6s	1.2V
7s	1V
8s	0.8V
9s	0.7V
10s	0.5V

Calculating, $R = t / [c \log (E/V)]$
 $= 1.043 \text{ M Ohm}$

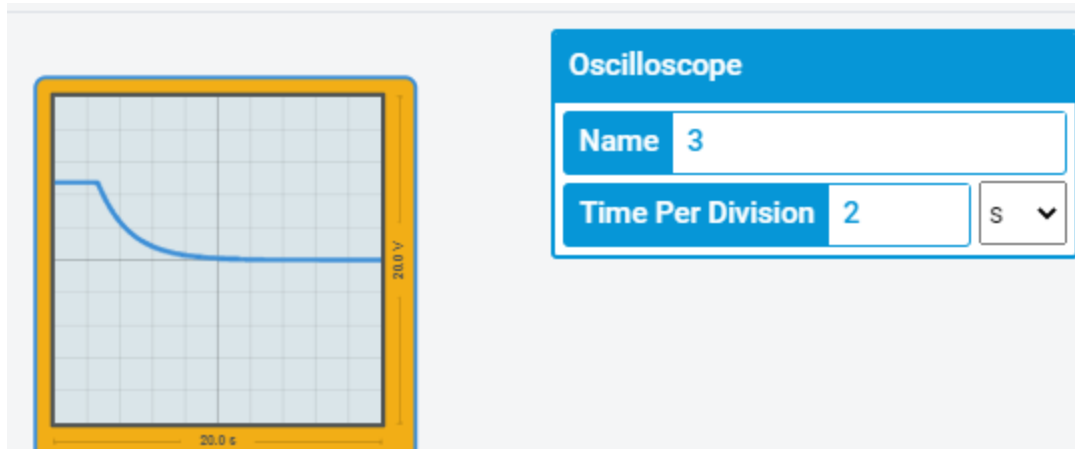CASE 3 (1 μ F , R = 2M Ohm, R1 = 100 k Ohm)




The Capacitor took almost 5s to discharge .

The following table was obtained :

Time	Voltage across C(V)
t=0s	4.54
1s	2.5
2s	1.5
3s	1
4s	0.6
5s	0.4
6s	0.2
7s	0.1
8s	50mV
9s	25mV
10s	0.05mV

Calculating, $R = t / [c \log (E/V)]$
= 2.01 M Ohm

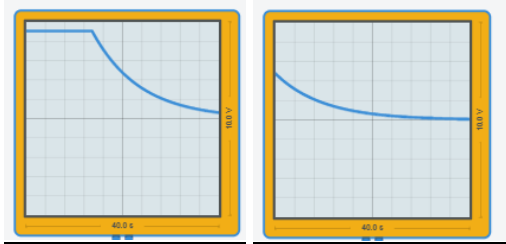CASE 4 (10uF , R = 2M Ohm, R1 = 100 k Ohm)




The Capacitor took almost 5s to discharge .

The following table was obtained :

Time	Voltage across C(V)
t=0s	4.54 V
2s	3.5 V
4s	3 V
6s	2.4 V
8s	2 V
10s	1.6V
12s	1.2V
14s	1V
16s	0.8V
18s	0.7V
20s	0.5V

Calculating, $R = t / [c \log (E/V)]$
 $= 2.086 \text{ M Ohm}$

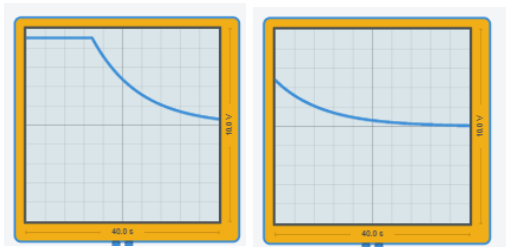CASE 5 (1uF , R = 4M Ohm, R1 = 100 k Ohm)



The Capacitor took almost 5s to discharge .


The following table was obtained :

Time	Voltage across C(V)
t=0s	4.54
2s	2.5
4s	1.5
6s	1
8s	0.6
10s	0.4
12s	0.2
14s	0.1
16s	50mV
18s	25mV
20s	0.05mV

Calculating, $R = t / [C \log (E/V)]$
 $= 4.003M \text{ Ohm}$

as it was more convenient to take the readings with more time per division, we took the reading upto 20 s

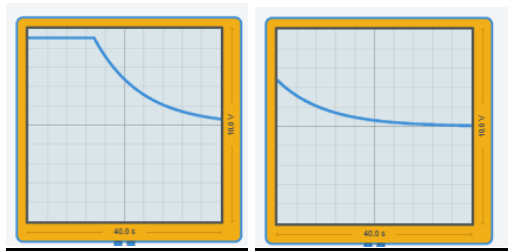CASE 6 (10uF , R = 4M Ohm, R1 = 100 k Ohm)



The Capacitor took almost 5s to discharge .


The following table was obtained :

Time	Voltage across C(V)
t=0s	4.54 V
4s	3.5 V
8s	3 V
12s	2.4 V
16s	2 V
20s	1.6V

24s	1.2V
28s	1V
32s	0.8V
36s	0.7V
40s	0.5V

Calculating, $R = t / [c \log (E/V)]$
 $= 4.0057M \text{ Ohm}$

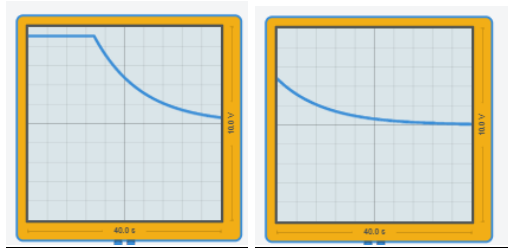CASE 7 (1uF , R = 10M Ohm, R1 = 100 k Ohm)



The Capacitor took almost 5s to discharge .

The following table was obtained :

Time	Voltage across C(V)
t=0s	4.54
5s	2.76
10s	1.25
15s	1
20s	0.5
25s	0.33
30s	0.25
35s	0.15
40s	75mV
45s	33mV
50s	0.075mV


Calculating, $R = t / [c \log (E/V)]$
 $= 10.455M \text{ Ohm}$

MATLAB CODE SIMULATION:

Code :

```
1 E = 12;  
2 R = 0.5e+6;  
3 C = 4.7e-6;  
4  
5 RC = R*C;  
6 tmax = 10;  
7 t = 0:0.01:tmax;  
8 N = tmax / 0.01;  
9 V = E*exp(-t/RC);  
10 subplot(2,1,1), plot (t,V);  
11 grid on  
12 title('High Resistance Measurement');  
13 xlabel('time(seconds)');  
14 ylabel('voltage across capacitor');  
15 subplot(2,1,2), plot(t,log(V));  
16 grid on  
17 xlabel('time(seconds)');  
18 ylabel('log_e V')  
19 Rx = 0.01*N/ (C*log(E/V(N+1)))  
20 |
```

Output :

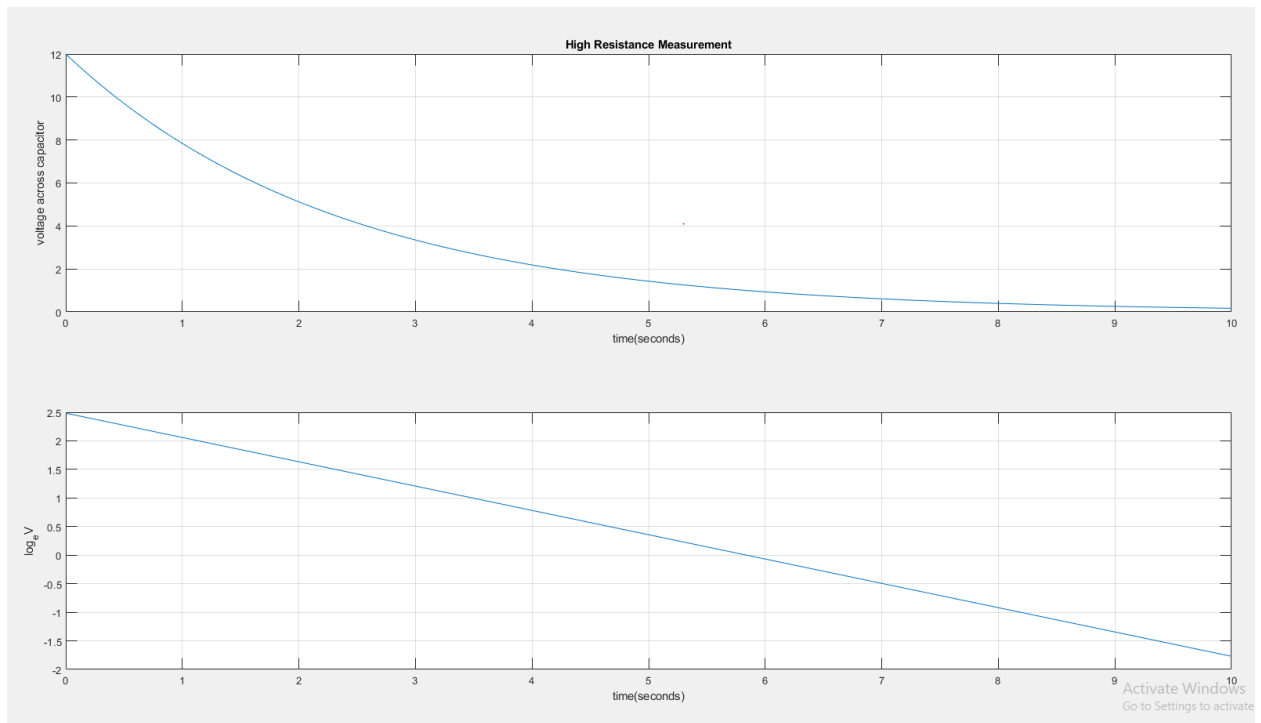


Alternative method Matlab code :

Code :

```
1 clear all; clc;
2 t = 0:0.01:10;
3 N = t(end)/ 0.01;
4 E = 12;
5 R = 1e6;
6 Rsw = 1e5;
7 C = 1e-6;
8 RC = R*C;
9 for i = 1:(N+1)
10     if (i <= 2/ 0.01)
11         V(i) = E;
12     elseif (i > 2/0.01)
13         Vinf = (R / (R + Rsw))*E ;
14         V(i) = Vinf + (E - Vinf)* exp (-(i - 2/0.01)/ (RC/0.01));
15     end
16 end
17 plot (t, V)
18 grid on
19 title('High resistance measurement');
20 xlabel('Time(seconds)');
21 ylabel('Voltage across capacitor');
22
23
```

Output :

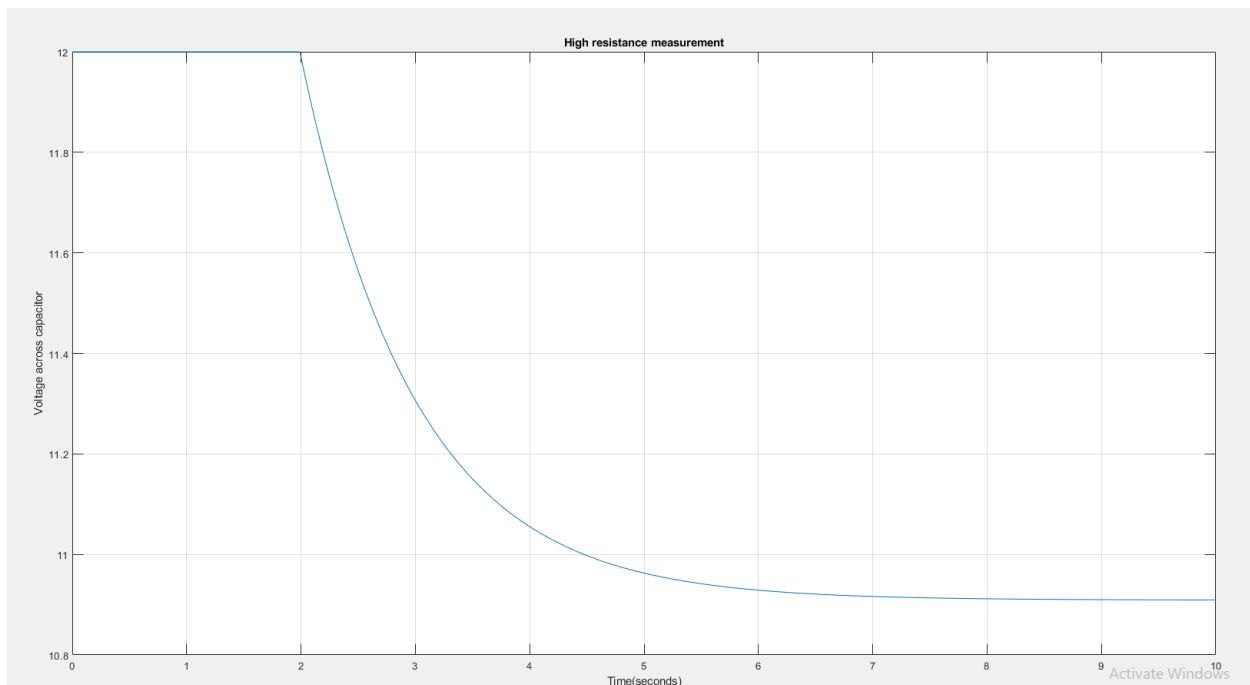

Discussion :

Observing the voltage discharge through the tinkercad oscilloscope was difficult and somewhat inaccurate. In order to make the process more convenient, as the circuits with greater capacitor values and the circuits with greater resistance values

require more time to descend, and discharge, the readings were taken longer than 10s to improve the accuracy of the system.